



**HACETTEPE**  
University

**VERILOG ASSIGNMENT 2**

**Name :** Muhammed Said

**Surname:** Kaya

**Student Number :** 21627428

**Section :** 02

**Subject :** Implementing Half Adder - 1 Bit Full Adder – 4 Bit Full Adder

## Module of Half Adder

```
`timescale 1ns / 1ps
```

```
module HalfAdder(
```

```
    output Sum,Carry,
```

```
    input A,B
```

```
);
```

```
xor(Sum,A,B);
```

```
and(Carry,A,B);
```

```
endmodule
```

## TestBench of Half Adder

```
`timescale 1ns / 1ps
```

```
module HalfAdder_TestBench;
```

```
// Inputs
```

```
    reg A;
```

```
    reg B;
```

```
// Outputs
```

```
    wire Sum;
```

```
    wire Carry;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
    HalfAdder uut (
```

```
        .Sum(Sum),
```

```
        .Carry(Carry),
```

```
        .A(A),
```

```
        .B(B)
```

```
);
```

```
    initial begin
```

```
        // Initialize Inputs
```

```
            A = 0;
```

```
            B = 0;
```

```
        // Wait 100 ns for global reset to finish
```

```
            #100;
```

```
        // Initialize Inputs
```

```
            A = 0;
```

```
            B = 1;
```

```
        // Wait 100 ns for global reset to finish
```

```
            #100;
```

```
        // Initialize Inputs
```

```
            A = 1;
```

```
            B = 0;
```

```
        // Wait 100 ns for global reset to finish
```

```
            #100;
```

```
        // Initialize Inputs
```

```
            A = 1;
```


```
            B = 1;
```

```
        // Add stimulus here
```

```
    end
```

```
endmodule
```

## Waveform of Half Adder

 

## Module of 1 Bit Adder

```
`timescale 1ns / 1ps
```

```
module HalfAdder( output Sum, output  
Carry, input A , input B );
```

```
    xor(Sum,A,B);  
    and(Carry,A,B);
```

```
endmodule
```

```
module OneBitFullAdder(
```

```
    output Carry,Sum,  
    input A,B,Cin
```

```
);
```

```
    wire sum1,carry1,carry2;
```

```
    HalfAdder ha1(sum1 ,carry1 ,A ,B);  
    HalfAdder ha2(Sum ,carry2 ,sum1
```

```
,Cin);
```

```
    or(Carry ,carry2 ,carry1);
```

```
endmodule
```

## TestBench Of 1 Bit Adder

```
`timescale 1ns / 1ps
```

```
module OneBitFullAdder_TestBench;
```

```
    // Inputs  
    reg A;  
    reg B;  
    reg Cin;
```

```
    // Outputs  
    wire Carry;  
    wire Sum;
```

```
    // Instantiate the Unit Under Test  
(UUT)  
    OneBitFullAdder uut (
```

```
        .Carry(Carry),  
        .Sum(Sum),  
        .A(A),  
        .B(B),  
        .Cin(Cin)
```

```
);
```

```
    initial begin
```

```
        // Initialize Inputs  
        A = 0;  
        B = 0;  
        Cin = 0;  
        // Wait 100 ns for global reset
```

```
    to finish
```

```
        #100;  
        // Initialize Inputs  
        A = 0;  
        B = 0;  
        Cin = 1;  
        // Wait 100 ns for global reset
```

```
    to finish
```

```
        #100;  
        // Initialize Inputs  
        A = 0;  
        B = 1;  
        Cin = 0;  
        // Wait 100 ns for global reset
```

```
    to finish
```

```
        #100;  
        // Initialize Inputs  
        A = 0;  
        B = 1;  
        Cin = 1;  
        // Wait 100 ns for global reset
```

```
    to finish
```

```
        #100;  
        // Initialize Inputs  
        A = 1;  
        B = 0;  
        Cin = 0;  
        // Wait 100 ns for global reset
```

```
    to finish
```


```
        #100;  
        // Initialize Inputs  
        A = 1;  
        B = 0;  
        Cin = 1;  
        // Wait 100 ns for global reset
```

```
    to finish
```

```
        #100;  
        // Initialize Inputs
```

	<b>A = 1;</b> <b>B = 1;</b> <b>Cin = 0;</b> <b>// Wait 100 ns for global reset</b>  <b>#100;</b> <b>// Initialize Inputs</b> <b>A = 1;</b> <b>B = 1;</b>		<b>Cin = 1;</b> <b>// Wait 100 ns for global reset</b>  <b>to finish</b>  <b>#100;</b> <b>// Add stimulus here</b>  <b>end</b>  <b>endmodule</b>
<b>to finish</b>			

Waveform of 1 Bit Full Adder

 

## Module Of 4 Bit Full Adder

```
`timescale 1ns / 1ps
```

```
module HalfAdder( output Sum, output  
Carry, input A , input B );
```

```
    xor(Sum,A,B);
```

```
    and(Carry,A,B);
```

```
endmodule
```

```
module OneBitFullAdder( output Carry,  
output Sum, input A, input B, input Cin );
```

```
    wire sum1,carry1,carry2;
```

```
    HalfAdder ha1(sum1 ,carry1 ,A ,B);
```

```
    HalfAdder ha2(Sum ,carry2 ,sum1  
,Cin);
```

```
    or(Carry ,carry2 ,carry1);
```

```
endmodule
```

```
module FourBitFullAdder(
```

```
    output [3:0]Sum,
```

```
    output Cout,
```

```
    input [3:0]A,B,
```

```
    input Cin
```

```
);
```

```
    wire carry1 , carry2 , carry3 ;
```

```
    OneBitFullAdder fa1(carry1 , Sum[0] ,  
A[0] , B[0] , Cin );
```

```
    OneBitFullAdder fa2(carry2 , Sum[1] ,  
A[1] , B[1] , carry1);
```

```
    OneBitFullAdder fa3(carry3 , Sum[2] ,  
A[2] , B[2] , carry2);
```

```
    OneBitFullAdder fa4(Cout , Sum[3] ,  
A[3] , B[3] , carry3);
```

```
endmodule
```

## TestBench Of 4 Bit Full Adder

```
`timescale 1ns / 1ps
```

```
module TestBench;
```

```
    // Inputs
```

```
    reg [3:0] A;
```

```
    reg [3:0] B;
```

```
    reg Cin;
```

```
    // Outputs
```

```
    wire [3:0] Sum;
```

```
    wire Cout;
```

```
    // Instantiate the Unit Under Test  
(UUT)
```

```
    FourBitFullAdder uut (
```


```
        .Sum(Sum),
```

```
        .Cout(Cout),
```


	.A(A),		// Wait 100 ns for global reset
	.B(B),	to finish	
	.Cin(Cin)		#100;
	);		// Initialize Inputs
			A = 4'b0000;
	initial begin		B = 4'b0101;
	// Initialize Inputs		Cin=0;
	A = 4'b1010;		// Wait 100 ns for global reset
	B = 4'b0101;	to finish	
	Cin=0;		#100;
	// Wait 100 ns for global reset		
to finish			// Add stimulus here
	#100;		
	// Initialize Inputs	end	
	A = 4'b1111;		
	B = 4'b0000;	endmodule	
	Cin=1;		
	// Wait 100 ns for global reset		
to finish			
	#100;		
	// Initialize Inputs		
	A = 4'b1111;		
	B = 4'b0001;		
	Cin=1;		
	// Wait 100 ns for global reset		
to finish			
	#100;		
	// Initialize Inputs		
	A = 4'b1111;		
	B = 4'b0101;		
	Cin=0;		




## Waveform of 4 Bit Full Adder

 

## RTL Schematic of 4 Bit Full Adder

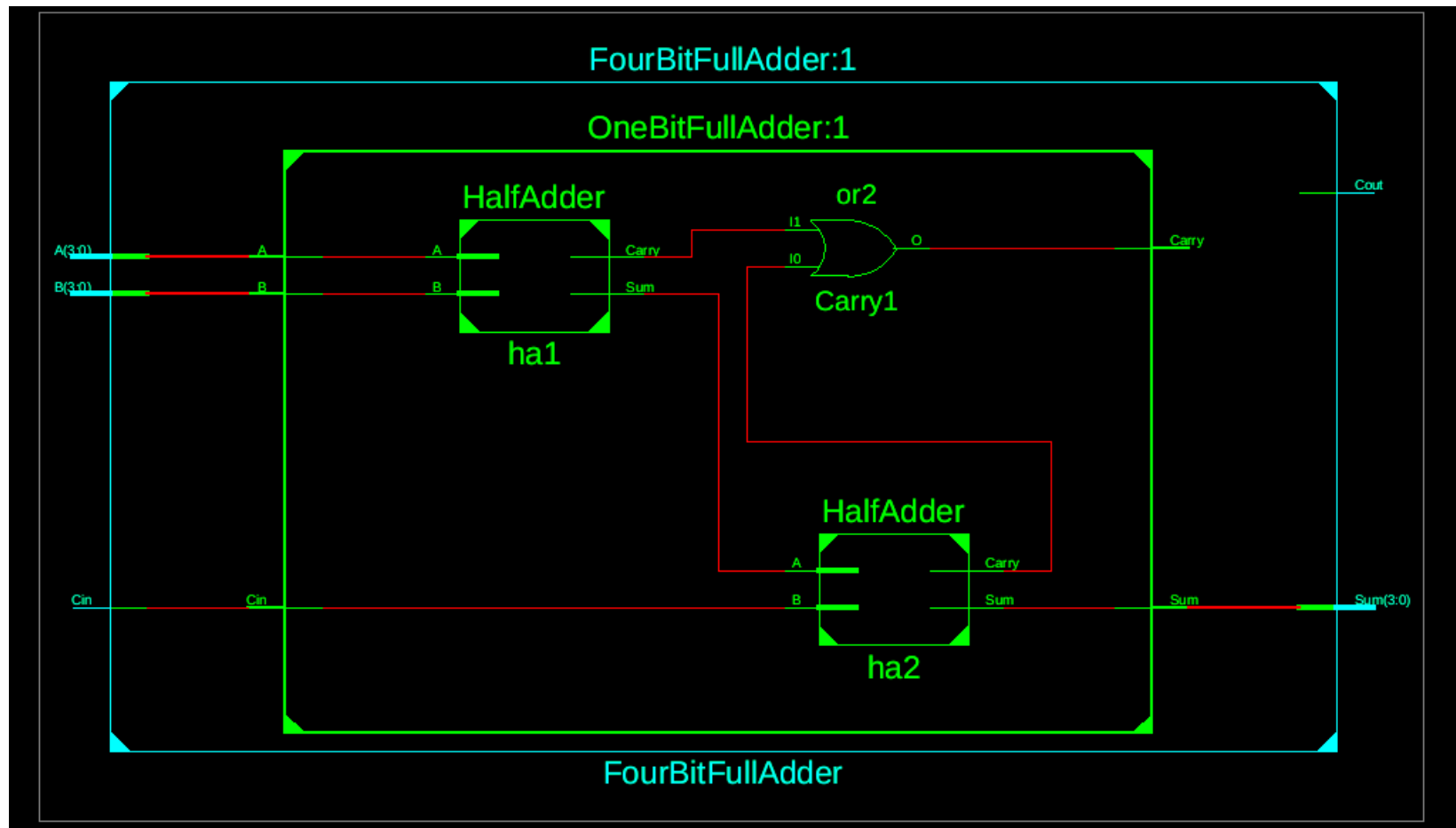

### RTL Schematic Of 1 Bit Full Adder

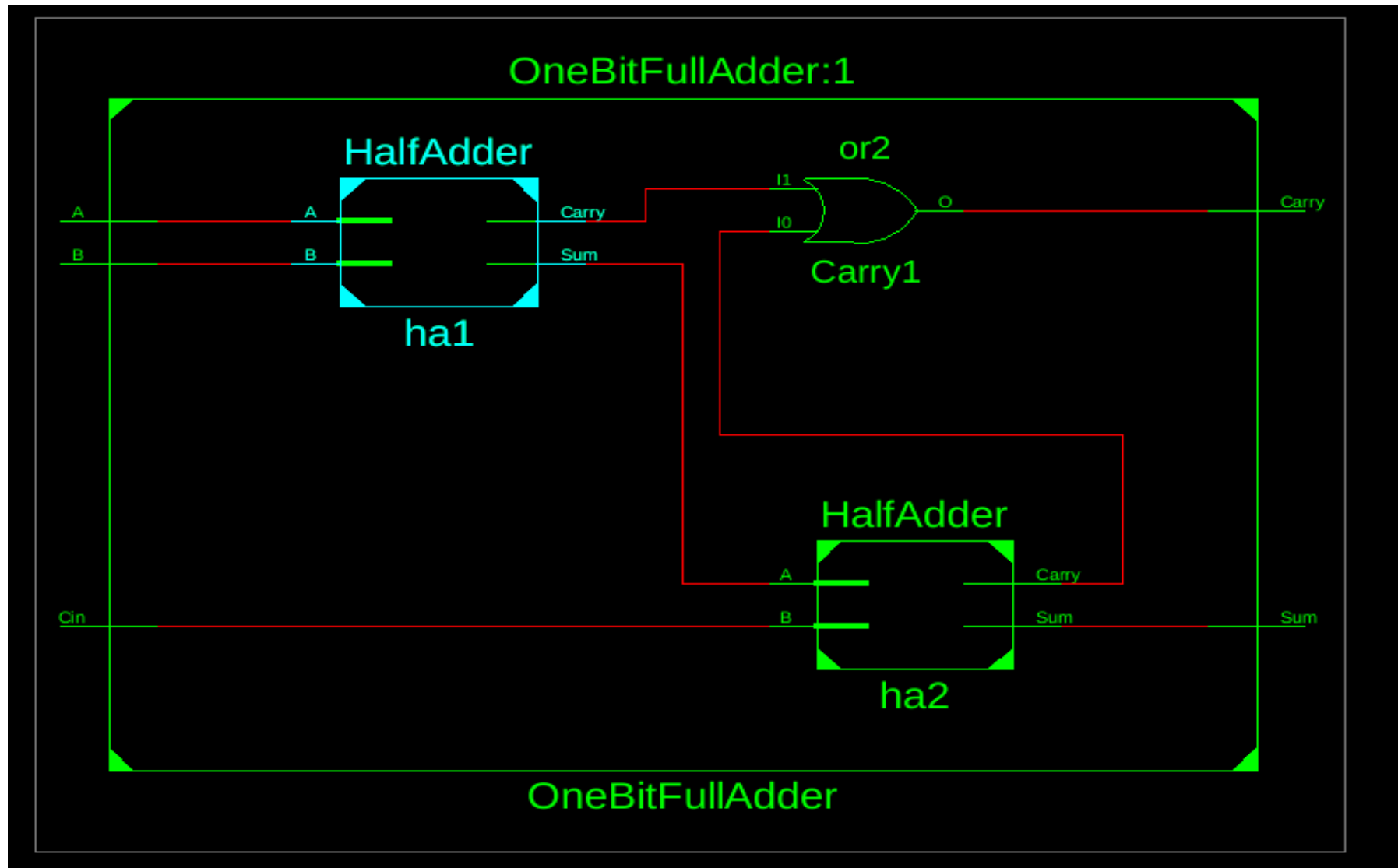

### RTL Schematic Of Half Adder

